NAND2TETRIS

Complete HDL Code Implementation, Logic Diagrams & Hardware Verification Report

Student Name Gurpreet Singh

Course: BTech CSE Cybersecurity / 3rd Sem

Roll Number 2501410028

Date: September 25, 2026

1. Introduction & Reflection on NAND Universality

In digital hardware architecture, functional completeness refers to a set of logical operators that can express all possible truth tables and Boolean functions. A single gate type capable of building any arbitrary logic function without requiring any other gate type is termed a universal gate. The NAND (NOT-AND) gate is a fundamental universal gate.

From a physical manufacturing perspective, implementing hardware exclusively using NAND gates provides immense advantages: it standardizes semiconductor fabrication, maximizes logic density on silicon dies, reduces propagation delay, and minimizes unit production costs. In the NAND2Tetris framework, we construct an entire 16-bit computer system from the ground up starting solely from primitive NAND logic.

Formal Proofs & Boolean Derivations from NAND Logic

- **NOT Gate (Inverter):** `NOT(a) = a NAND a` — Since a NAND a = NOT(a AND a) = NOT(a).
- **AND Gate:** `AND(a, b) = NOT(a NAND b) = (a NAND b) NAND (a NAND b)` — An AND gate is derived by passing the output of a NAND gate through a NAND-based inverter.
- **OR Gate:** `OR(a, b) = NOT(a) NAND NOT(b) = (a NAND a) NAND (b NAND b)` — Applying De Morgan's Theorem: NOT(NOT(a) AND NOT(b)) = a OR b.
- **XOR Gate (Exclusive OR):** `XOR(a, b) = (a OR b) AND NOT(a AND b)` — Constructed via fundamental NAND nodes: let w1 = a NAND b, w2 = a NAND w1, w3 = b NAND w1; then XOR = w2 NAND w3.

2. Project 1 & 2 Chip-by-Chip Implementations


2.1 Chip: NOT Gate (Not.hdl)

- **Function:** Inverts a 1-bit input signal.
- **Interface:** Inputs: in (1-bit) | Outputs: out (1-bit)


```
CHIP Not {
    IN in;
    OUT out;

    PARTS:
    Nand(a=in, b=in, out=out);
}
```

[Logic Diagram]

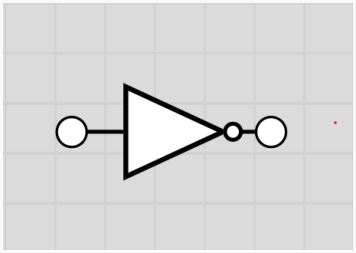

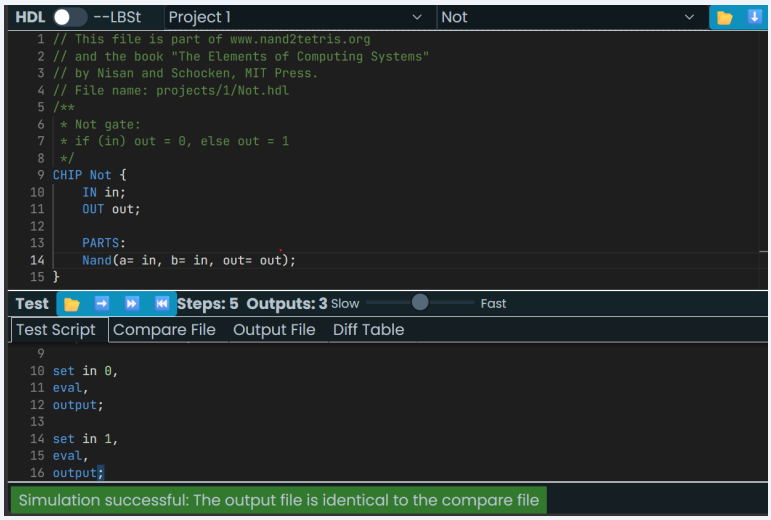[PASS Hardware Simulator Screenshot for NOT Gate]




2.2 Chip: AND Gate (And.hdl)

- **Function:** Outputs 1 if both inputs a and b are 1, else 0.
- **Interface:** Inputs: a, b (1-bit) | Outputs: out (1-bit)


```
CHIP And {
    IN a, b;
    OUT out;

    PARTS:
    Nand(a=a, b=b, out=c);
    Not(in=c, out=out);
}
```

[Logic Diagram]

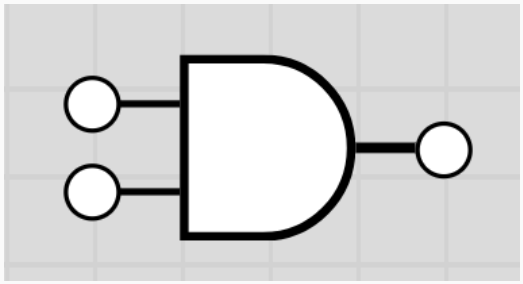

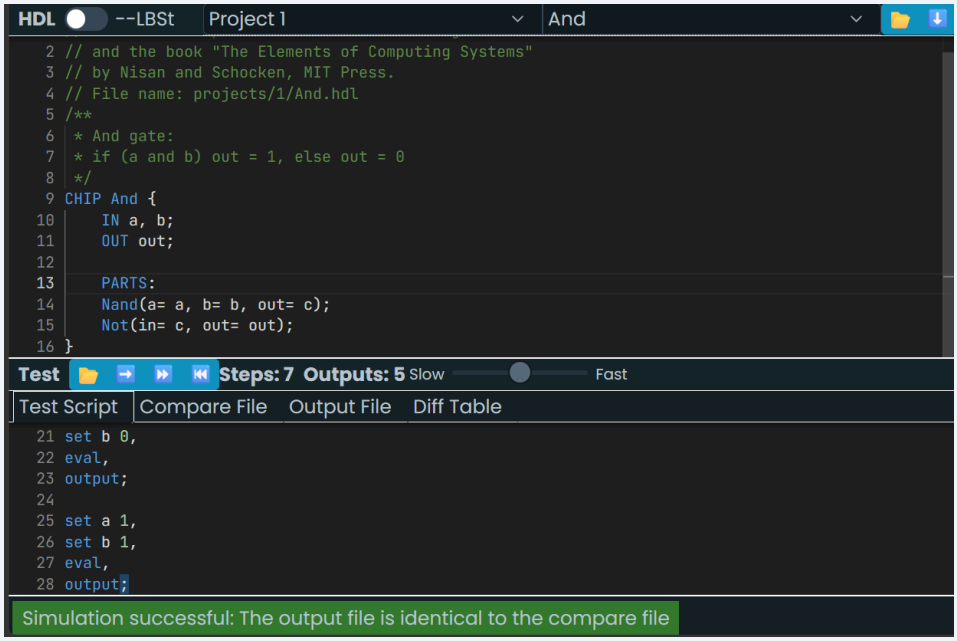[PASS Hardware Simulator Screenshot for AND Gate]




2.3 Chip: OR Gate (Or.hdl)

- **Function:** Outputs 1 if at least one input is 1.
- **Interface:** Inputs: a, b (1-bit) | Outputs: out (1-bit)


```
CHIP Or {
    IN a, b;
    OUT out;

    PARTS:
    Not(a=a, b=a, out=x);
    Not(a=b, b=b, out=y);
    Nand(a=x, b=y, out=out);
}
```

[Logic Diagram]

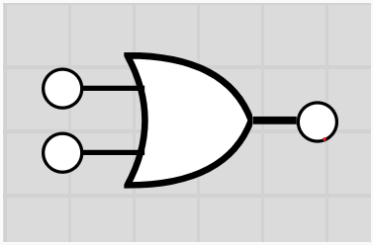

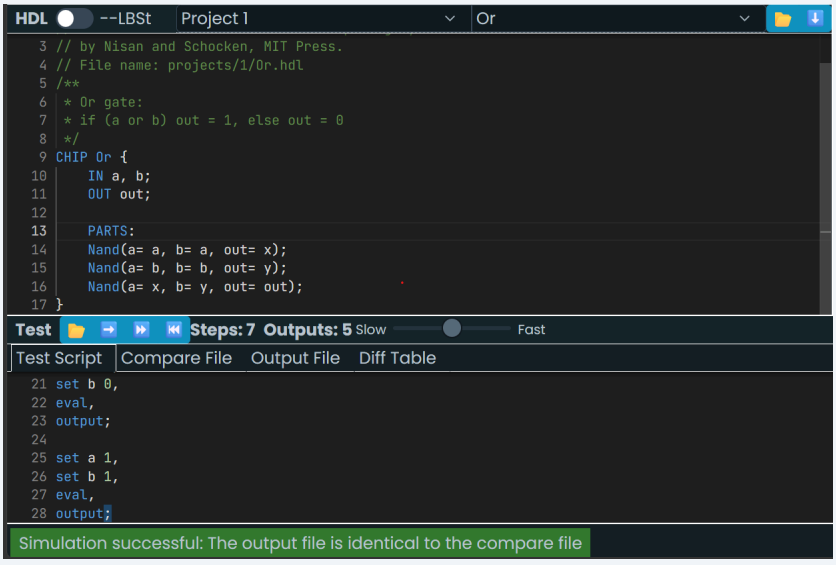[PASS Hardware Simulator Screenshot for OR Gate]




2.4 Chip: XOR Gate (Xor.hdl)

- **Function:** Exclusive OR: Outputs 1 if exactly one input is 1.
- **Interface:** Inputs: a, b (1-bit) | Outputs: out (1-bit)


```
CHIP Xor {
    IN a, b;
    OUT out;

    PARTS:
    Nand(a=a, b=b, out=x);
    Nand(a=a, b=x, out=y);
    Nand(a=b, b=x, out=z);
    Nand(a=y, b=z, out=out);
}
```

[Logic Diagram]

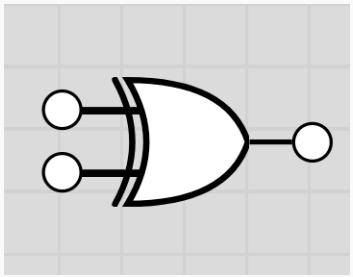

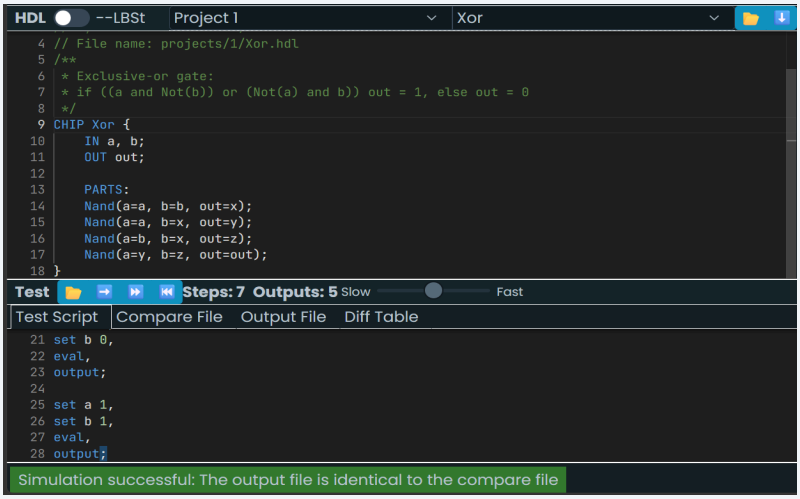[PASS Hardware Simulator Screenshot for XOR Gate]




2.5 Chip: Multiplexer (Mux.hdl)

- **Function:** 2-to-1 Multiplexer: Outputs 'a' if sel==0, 'b' if sel==1.
- **Interface:** Inputs: a, b, sel (1-bit) | Outputs: out (1-bit)


```
CHIP Mux {
    IN a, b, sel;
    OUT out;

    PARTS:
    Not(in=sel, out=nsel);
    And(a=a, b=nsel, out=x);
    And(a=b, b=sel, out=y);
    Or(a=x, b=y, out=out);
}
```

[Logic Diagram]

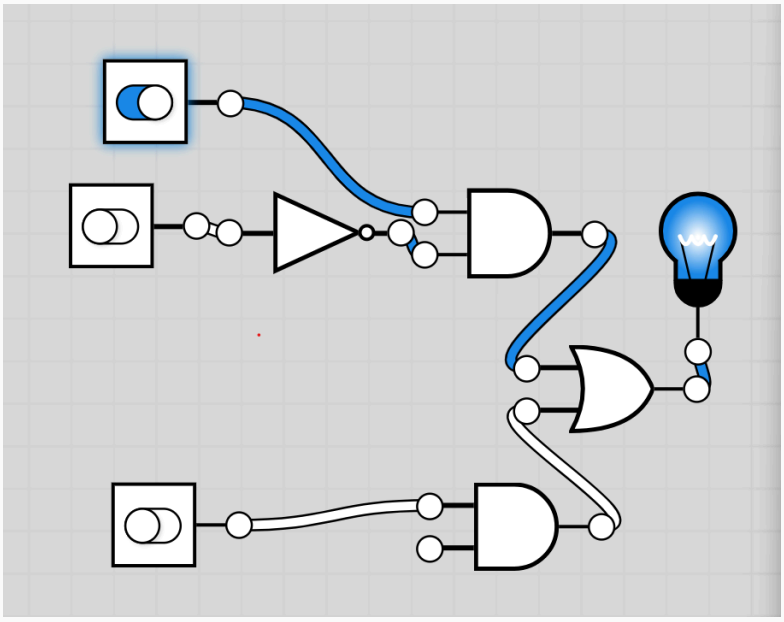

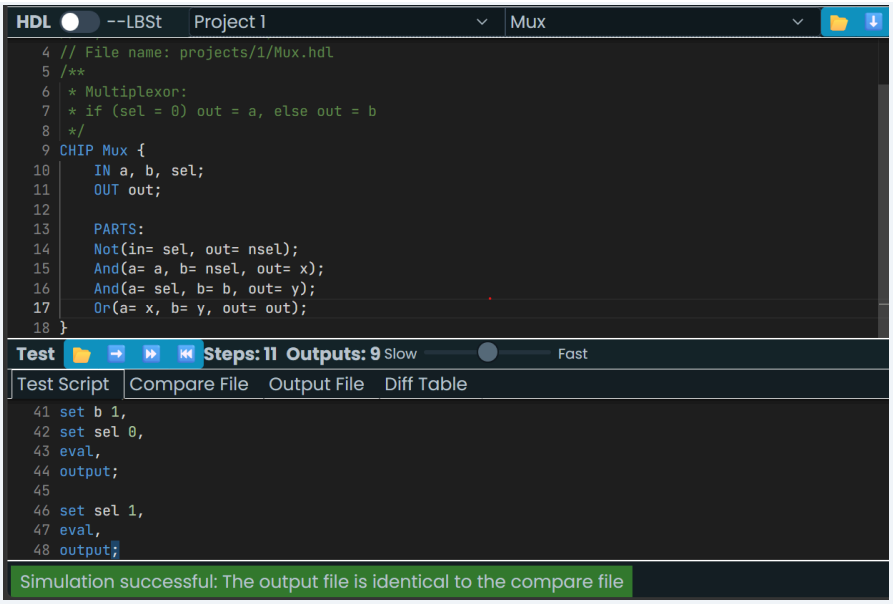[PASS Hardware Simulator Screenshot for Mux Gate]




2.6 Chip: Demultiplexer (DMux.hdl)

- **Function:** 1-to-2 Demultiplexer: Routes 'in' to {a,0} if sel==0, or {0,b} if sel==1.
- **Interface:** Inputs: in, sel (1-bit) | Outputs: a, b (1-bit)


```
CHIP DMux {
    IN in, sel;
    OUT a, b;

    PARTS:
    Not(in=sel, out=nsel);
    And(a=in, b=nsel, out=a);
    And(a=in, b=sel, out=b);
}
```

[Logic Diagram]

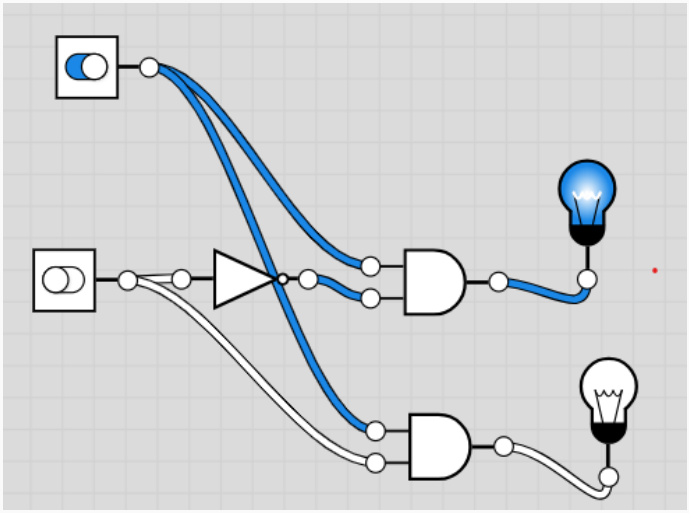

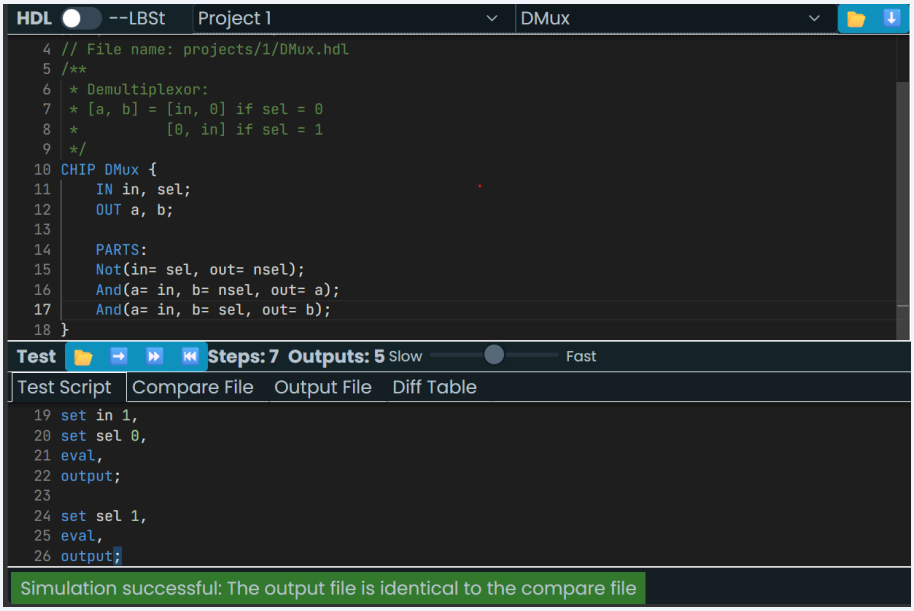[PASS Hardware Simulator Screenshot for DMux Gate]



2.7 Chip: 16-Bit Bitwise NOT (Not16.hdl)


- **Function:** Applies NOT logic individually to 16 input bits.
- **Interface:** Inputs: in[16] | Outputs: out[16]

```
CHIP Not16 {
    IN in[16];
```


```
    OUT out[16];

    PARTS:
    Not(in=in[0], out=out[0]);
    Not(in=in[1], out=out[1]);
    Not(in=in[2], out=out[2]);
    Not(in=in[3], out=out[3]);
    Not(in=in[4], out=out[4]);
    Not(in=in[5], out=out[5]);
    Not(in=in[6], out=out[6]);
    Not(in=in[7], out=out[7]);
    Not(in=in[8], out=out[8]);
    Not(in=in[9], out=out[9]);
    Not(in=in[10], out=out[10]);
    Not(in=in[11], out=out[11]);
    Not(in=in[12], out=out[12]);
    Not(in=in[13], out=out[13]);
    Not(in=in[14], out=out[14]);
    Not(in=in[15], out=out[15]);
}
```

[Logic Diagram]

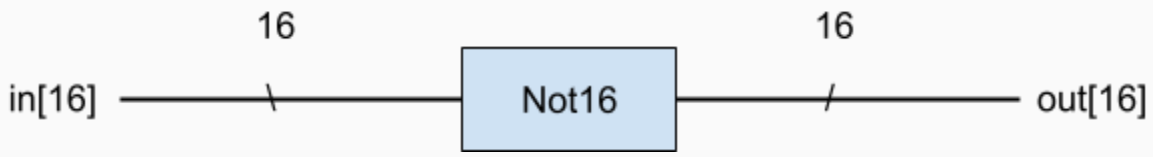

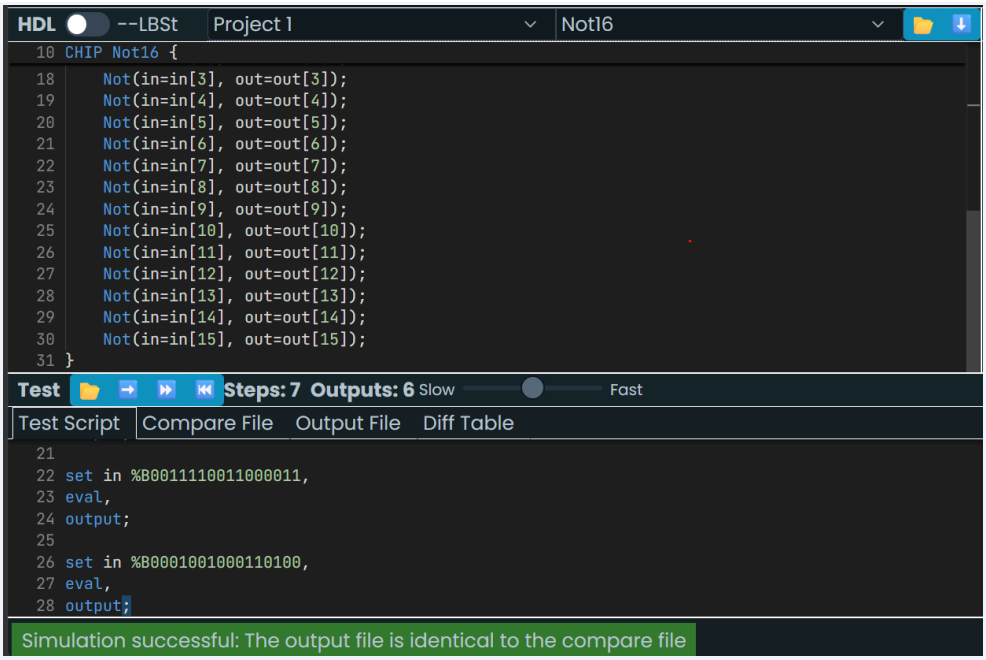[PASS Hardware Simulator Screenshot for Not16 Gate]




2.8 Chip: 16-Bit Bitwise AND (And16.hdl)

- **Function:** Applies AND logic individually across two 16-bit buses.
- **Interface:** Inputs: a[16], b[16] | Outputs: out[16]


```
CHIP And16 {
    IN a[16], b[16];
    OUT out[16];

    PARTS:
    And(a=a[0], b=b[0], out=out[0]);
    And(a=a[1], b=b[1], out=out[1]);
    And(a=a[2], b=b[2], out=out[2]);
    And(a=a[3], b=b[3], out=out[3]);
    And(a=a[4], b=b[4], out=out[4]);
    And(a=a[5], b=b[5], out=out[5]);
    And(a=a[6], b=b[6], out=out[6]);
    And(a=a[7], b=b[7], out=out[7]);
    And(a=a[8], b=b[8], out=out[8]);
    And(a=a[9], b=b[9], out=out[9]);
    And(a=a[10], b=b[10], out=out[10]);
    And(a=a[11], b=b[11], out=out[11]);
    And(a=a[12], b=b[12], out=out[12]);
    And(a=a[13], b=b[13], out=out[13]);
    And(a=a[14], b=b[14], out=out[14]);
    And(a=a[15], b=b[15], out=out[15]);
}
```

[Logic Diagram]

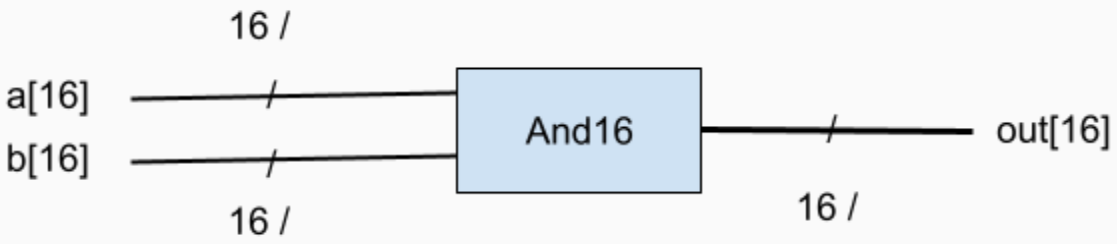

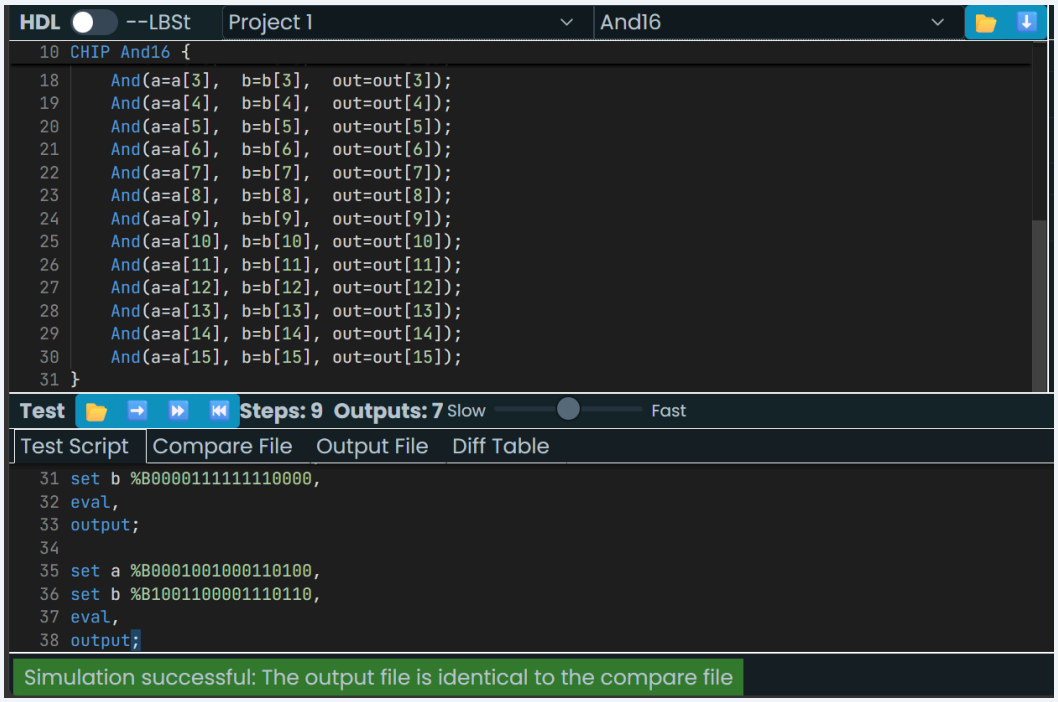[PASS Hardware Simulator Screenshot for And16 Gate]




2.9 Chip: 16-Bit Bitwise OR (Or16.hdl)

- **Function:** Applies OR logic individually across two 16-bit buses.
- **Interface:** Inputs: a[16], b[16] | Outputs: out[16]


```
CHIP Or16 {
    IN a[16], b[16];
    OUT out[16];

    PARTS:
    Or(a=a[0], b=b[0], out=out[0]);
    Or(a=a[1], b=b[1], out=out[1]);
    Or(a=a[2], b=b[2], out=out[2]);
    Or(a=a[3], b=b[3], out=out[3]);
    Or(a=a[4], b=b[4], out=out[4]);
    Or(a=a[5], b=b[5], out=out[5]);
    Or(a=a[6], b=b[6], out=out[6]);
    Or(a=a[7], b=b[7], out=out[7]);
    Or(a=a[8], b=b[8], out=out[8]);
    Or(a=a[9], b=b[9], out=out[9]);
    Or(a=a[10], b=b[10], out=out[10]);
    Or(a=a[11], b=b[11], out=out[11]);
    Or(a=a[12], b=b[12], out=out[12]);
    Or(a=a[13], b=b[13], out=out[13]);
    Or(a=a[14], b=b[14], out=out[14]);
    Or(a=a[15], b=b[15], out=out[15]);
}
```

[Logic Diagram]

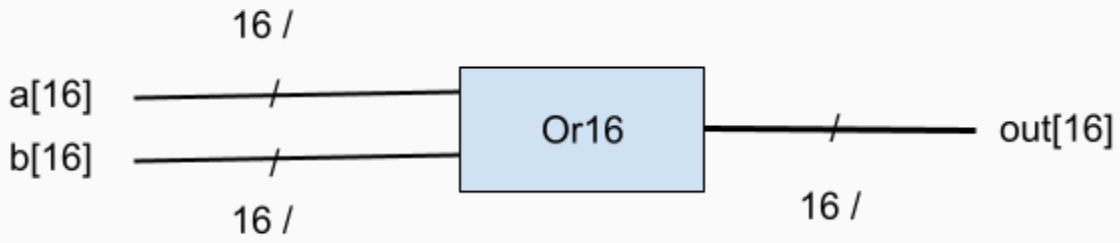

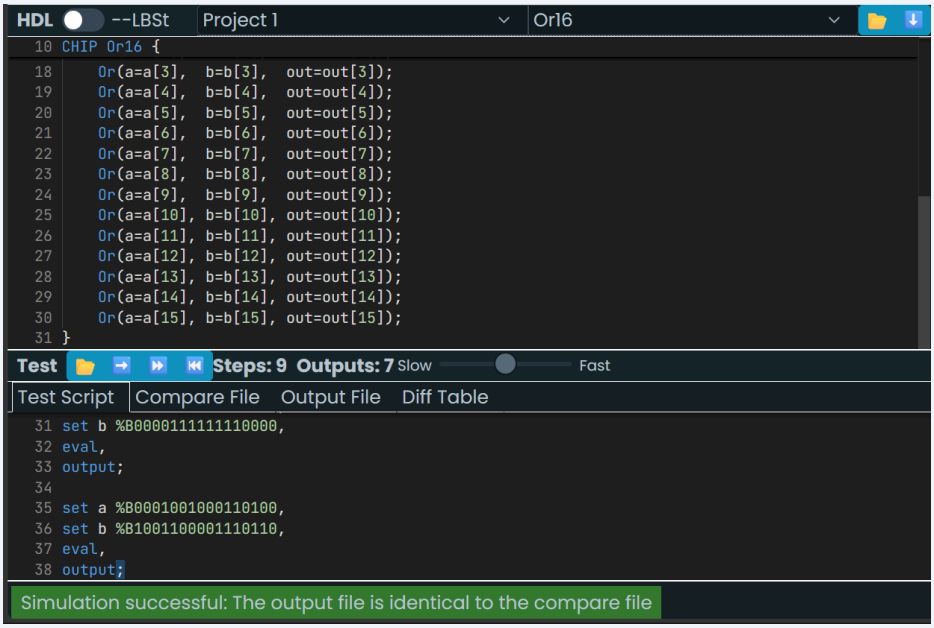[PASS Hardware Simulator Screenshot for Or16 Gate]




2.10 Chip: 16-Bit 2-to-1 Multiplexer (Mux16.hdl)

- **Function:** Selects between two 16-bit buses based on sel.
- **Interface:** Inputs: a[16], b[16], sel | Outputs: out[16]

```
CHIP Mux16 {
    IN a[16], b[16], sel;
    OUT out[16];

    PARTS:
    Mux(a=a[0], b=b[0], sel=sel, out=out[0]);
    Mux(a=a[1], b=b[1], sel=sel, out=out[1]);
    Mux(a=a[2], b=b[2], sel=sel, out=out[2]);
    Mux(a=a[3], b=b[3], sel=sel, out=out[3]);
    Mux(a=a[4], b=b[4], sel=sel, out=out[4]);
    Mux(a=a[5], b=b[5], sel=sel, out=out[5]);
    Mux(a=a[6], b=b[6], sel=sel, out=out[6]);
    Mux(a=a[7], b=b[7], sel=sel, out=out[7]);
    Mux(a=a[8], b=b[8], sel=sel, out=out[8]);
    Mux(a=a[9], b=b[9], sel=sel, out=out[9]);
    Mux(a=a[10], b=b[10], sel=sel, out=out[10]);
    Mux(a=a[11], b=b[11], sel=sel, out=out[11]);
    Mux(a=a[12], b=b[12], sel=sel, out=out[12]);
    Mux(a=a[13], b=b[13], sel=sel, out=out[13]);
    Mux(a=a[14], b=b[14], sel=sel, out=out[14]);
    Mux(a=a[15], b=b[15], sel=sel, out=out[15]);
}
```

[Logic Diagram]

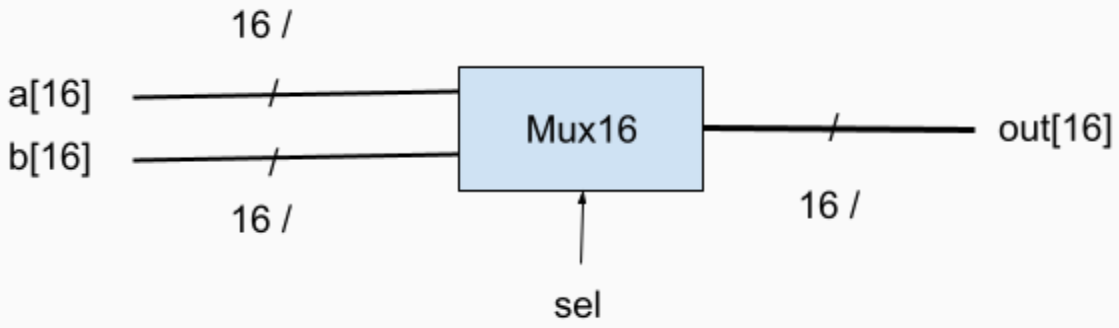

[PASS Hardware Simulator Screenshot for Mux16 Gate]

HDL --LBSt Project 1 Mux16

```
10 CHIP Mux16 {
18     Mux(a=a[3],  b=b[3],  sel=sel, out=out[3]);
19     Mux(a=a[4],  b=b[4],  sel=sel, out=out[4]);
20     Mux(a=a[5],  b=b[5],  sel=sel, out=out[5]);
21     Mux(a=a[6],  b=b[6],  sel=sel, out=out[6]);
22     Mux(a=a[7],  b=b[7],  sel=sel, out=out[7]);
23     Mux(a=a[8],  b=b[8],  sel=sel, out=out[8]);
24     Mux(a=a[9],  b=b[9],  sel=sel, out=out[9]);
25     Mux(a=a[10], b=b[10], sel=sel, out=out[10]);
26     Mux(a=a[11], b=b[11], sel=sel, out=out[11]);
27     Mux(a=a[12], b=b[12], sel=sel, out=out[12]);
28     Mux(a=a[13], b=b[13], sel=sel, out=out[13]);
29     Mux(a=a[14], b=b[14], sel=sel, out=out[14]);
30     Mux(a=a[15], b=b[15], sel=sel, out=out[15]);
31 }
```

Test Steps: 11 Outputs: 9 Slow Fast

Test Script | Compare File | Output File | Diff Table

```
41 set b %B0101010101010101,
42 set sel 0,
43 eval,
44 output;
45
46 set sel 1,
47 eval,
48 output;
```

Simulation successful: The output file is identical to the compare file


2.11 Chip: 8-Way OR Gate (Or8Way.hdl)

- **Function:** Outputs 1 if any of the 8 input bits is 1.
- **Interface:** Inputs: in[8] | Outputs: out (1-bit)


```
CHIP Or8Way {
    IN in[8];
    OUT out;

    PARTS:
    Or(a=in[0], b=in[1], out=o1);
    Or(a=o1, b=in[2], out=o2);
    Or(a=o2, b=in[3], out=o3);
    Or(a=o3, b=in[4], out=o4);
    Or(a=o4, b=in[5], out=o5);
    Or(a=o5, b=in[6], out=o6);
    Or(a=o6, b=in[7], out=out);
}
```

[Logic Diagram]

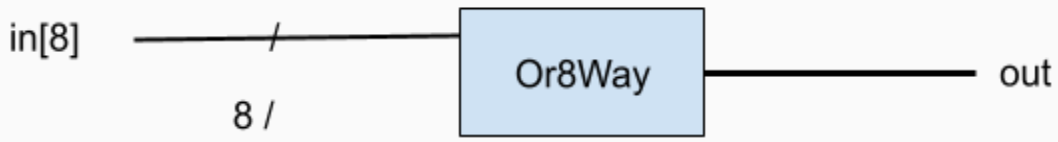

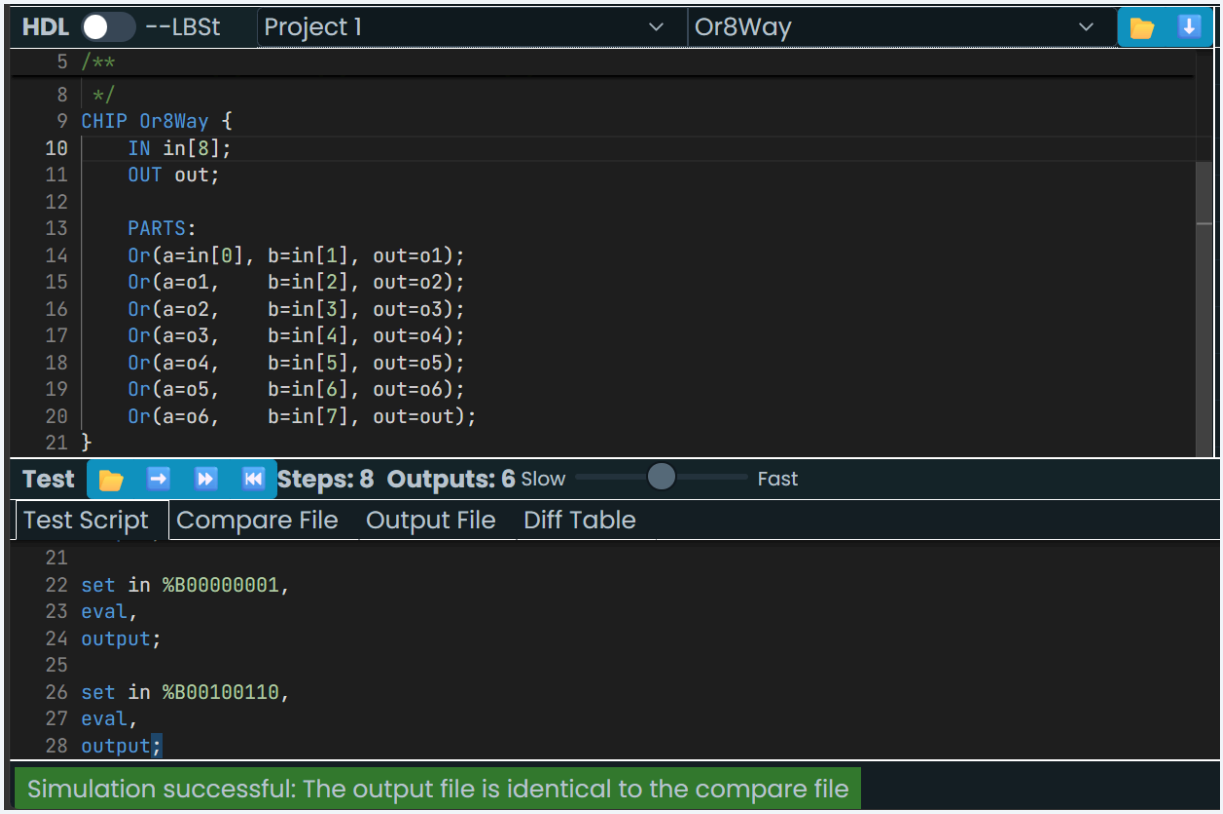[PASS Hardware Simulator Screenshot for Or8Way Gate]




2.12 Chip: 4-Way 16-Bit Multiplexer (Mux4Way16.hdl)

- **Function:** Selects between 4 16-bit buses using a 2-bit sel signal.
- **Interface:** Inputs: a[16], b[16], c[16], d[16], sel[2] | Outputs: out[16]

```
CHIP Mux4Way16 {
    IN a[16], b[16], c[16], d[16], sel[2];
    OUT out[16];

    PARTS:
    Mux16(a=a, b=b, sel=sel[0], out=ab);
    Mux16(a=c, b=d, sel=sel[0], out=cd);
    Mux16(a=ab, b=cd, sel=sel[1], out=out);
}
```

[Logic Diagram]

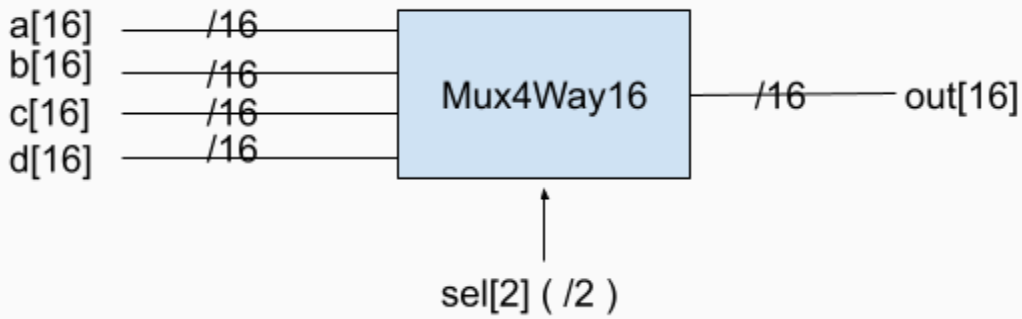

[PASS Hardware Simulator Screenshot for Mux4Way16 Gate]

HDL --LBSt Project 1 Mux4Way16

```
/**
 * out = a if sel = 00
 *       b if sel = 01
 *       c if sel = 10
 *       d if sel = 11
 */
CHIP Mux4Way16 {
    IN a[16], b[16], c[16], d[16], sel[2];
    OUT out[16];

    PARTS:
    Mux16(a=a, b=b, sel=sel[0], out=ab);
    Mux16(a=c, b=d, sel=sel[0], out=cd);
    Mux16(a=ab, b=cd, sel=sel[1], out=out);
}
```

Test Steps: 11 Outputs: 9 Slow Fast

Test Script | Compare File | Output File | Diff Table

```
set sel 2,
eval,
output;

set sel 3,
eval,
output;
```

Simulation successful: The output file is identical to the compare file

2.13 Chip: 8-Way 16-Bit Multiplexer (Mux8Way16.hdl)

- **Function:** Selects between 8 16-bit buses using a 3-bit sel signal.
- **Interface:** Inputs: a..h[16], sel[3] | Outputs: out[16]


```
CHIP Mux8Way16 {
    IN a[16], b[16], c[16], d[16], e[16], f[16], g[16], h[16], sel[3];
    OUT out[16];

    PARTS:
    Mux16(a=a, b=b, sel=sel[0], out=ab);
    Mux16(a=c, b=d, sel=sel[0], out=cd);
    Mux16(a=e, b=f, sel=sel[0], out=ef
    Mux16(a=g, b=h, sel=sel[0], out=gh);


    Mux16(a=ab. b=cd, sel=sel[1], out=abcd);
    Mux16(a=ef, b=gh, sel=sel[1], out=efgh);

    Mux16(a=abcd, b=efgh, sel=sel[2], out=out);
}
```

[Logic Diagram]

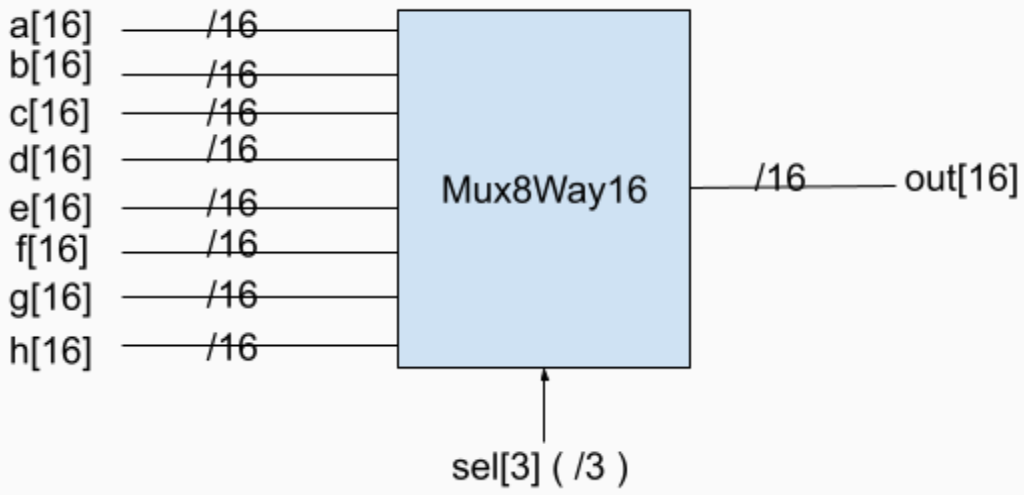

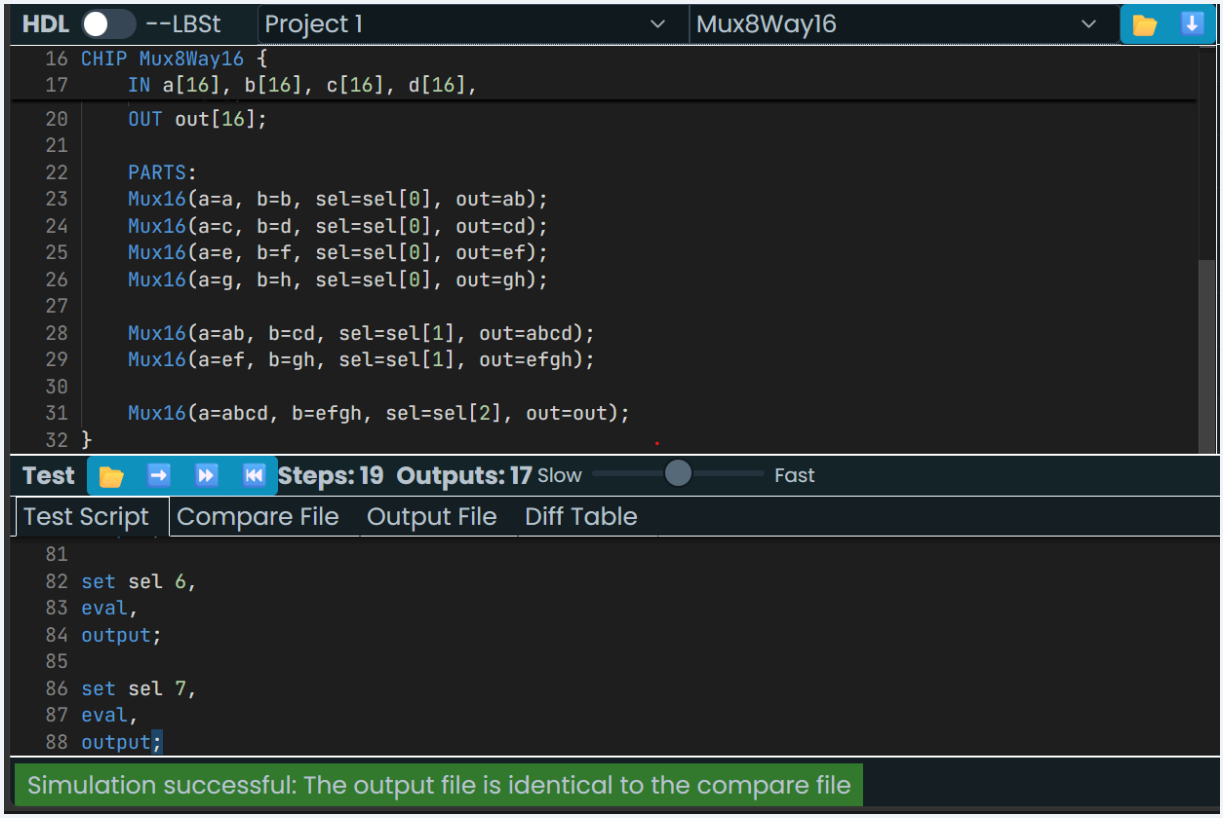[PASS Hardware Simulator Screenshot for Mux8Way16 Gate]



2.14 Chip: 4-Way 1-Bit Demultiplexer (DMux4Way.hdl)


- **Function:** Routes 1-bit input to one of 4 channels based on sel[2].
- **Interface:** Inputs: in, sel[2] | Outputs: a, b, c, d

```
CHIP DMux4Way {
    IN in, sel[2];
    OUT a, b, c, d;

    PARTS:
    DMux(in=in, sel=sel[1], a=top, b=bottom);

    DMux(in=top, sel=sel[0], a=a, b=b);
    DMux(in=bottom, sel=sel[0], a=c, b=d);
}
```

[Logic Diagram]

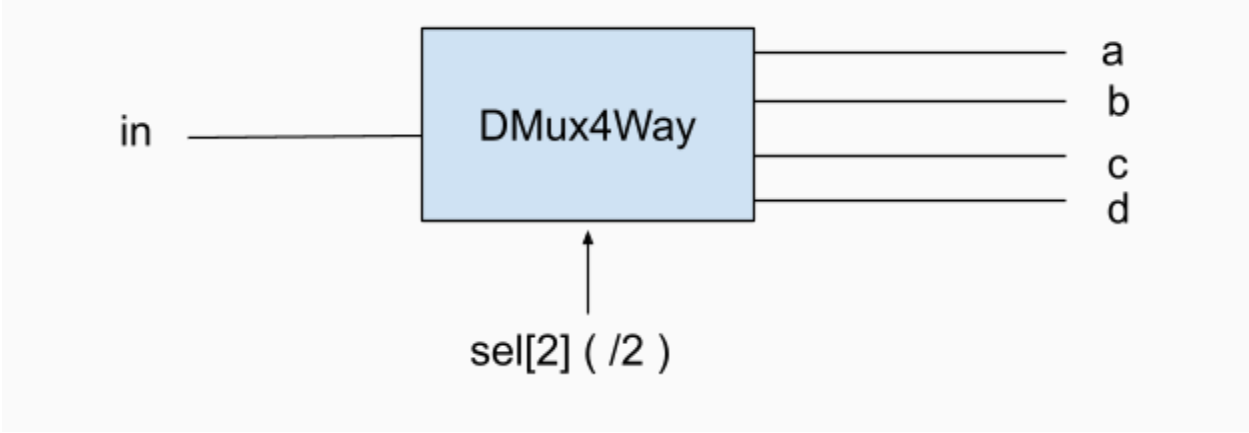

[PASS Hardware Simulator Screenshot for DMux4Way Gate]

HDL --LBSt Project 1 DMux4Way

```
/**
 *                [0, in, 0, 0] if sel = 01
 *                [0, 0, in, 0] if sel = 10
 *                [0, 0, 0, in] if sel = 11
 */
CHIP DMux4Way {
    IN in, sel[2];
    OUT a, b, c, d;

    PARTS:
    DMux(in=in, sel=sel[1], a=top, b=bottom);

    DMux(in=top,    sel=sel[0], a=a, b=b);
    DMux(in=bottom, sel=sel[0], a=c, b=d);
}
```

Test Steps: 11 Outputs: 9 Slow Fast

Test Script | Compare File | Output File | Diff Table

```
set sel %B10,
eval,
output;

set sel %B11,
eval,
output;
```

Simulation successful: The output file is identical to the compare file

2.15 Chip: 8-Way 1-Bit Demultiplexer (DMux8Way.hdl)


- **Function:** Routes 1-bit input to one of 8 channels based on sel[3].
- **Interface:** Inputs: in, sel[3] | Outputs: a, b, c, d, e, f, g, h

```
CHIP DMux8Way {
    IN in, sel[3];
    OUT a, b, c, d, e, f, g, h;


    PARTS:
    DMux(in=in, sel=sel[2], a=x, b=y);

    DMux4Way(in=x, sel=sel[0..1], a=a, b=b, c=c, d=d);
    DMux4Way(in=y, sel=sel[0..1], a=e, b=f, c=g, d=h);
}
```

[Logic Diagram]

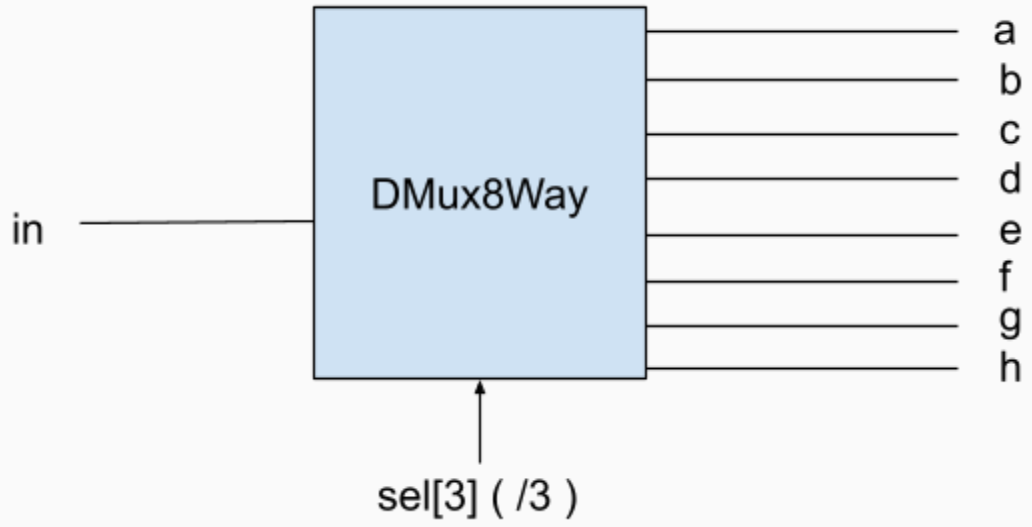

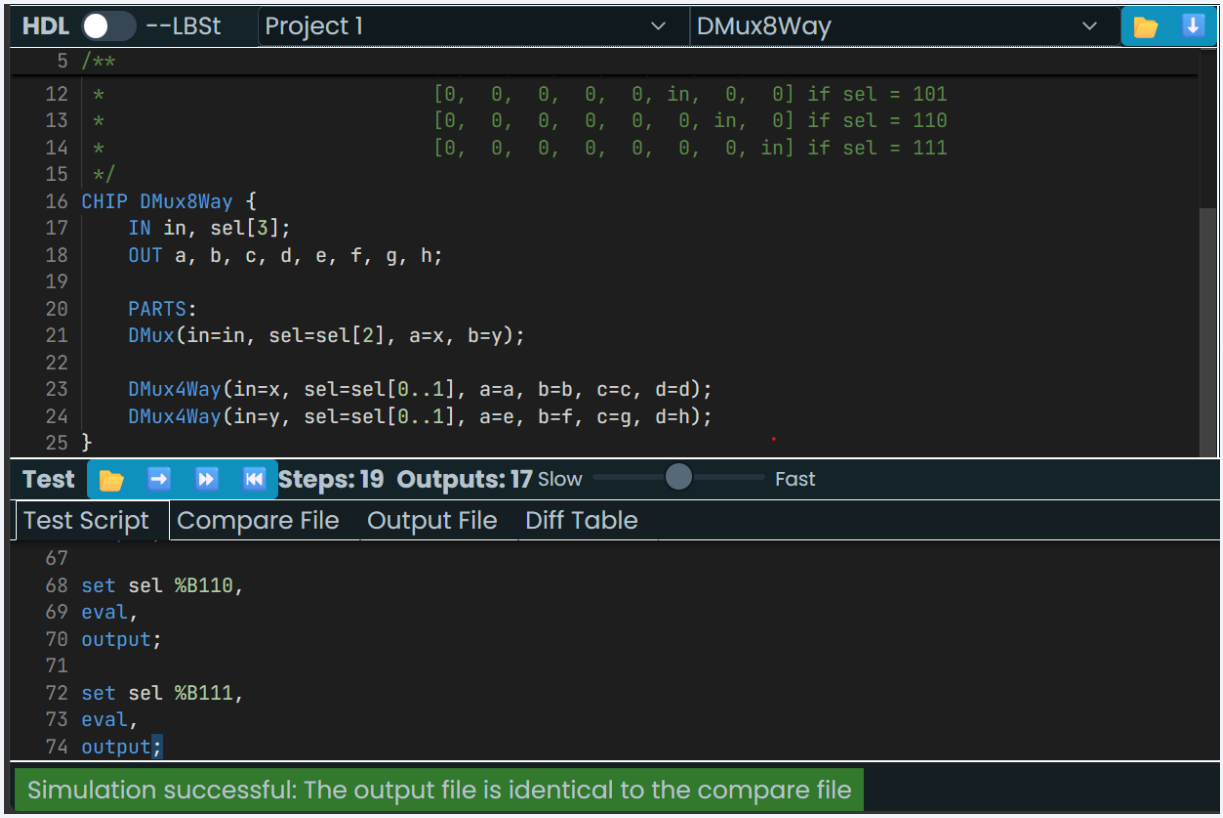[PASS Hardware Simulator Screenshot for DMux8Way Gate]




2.16 Chip: Half Adder (HalfAdder.hdl)

- **Function:** Adds two 1-bit values, producing sum and carry bits.
- **Interface:** Inputs: a, b (1-bit) | Outputs: sum, carry (1-bit)

```
CHIP HalfAdder {
    IN a, b;
    OUT sum, carry;

    PARTS:
    Xor(a=a, b=b, out=sum);
    And(a=a, b=b, out=carry);
}
```

[Logic Diagram]

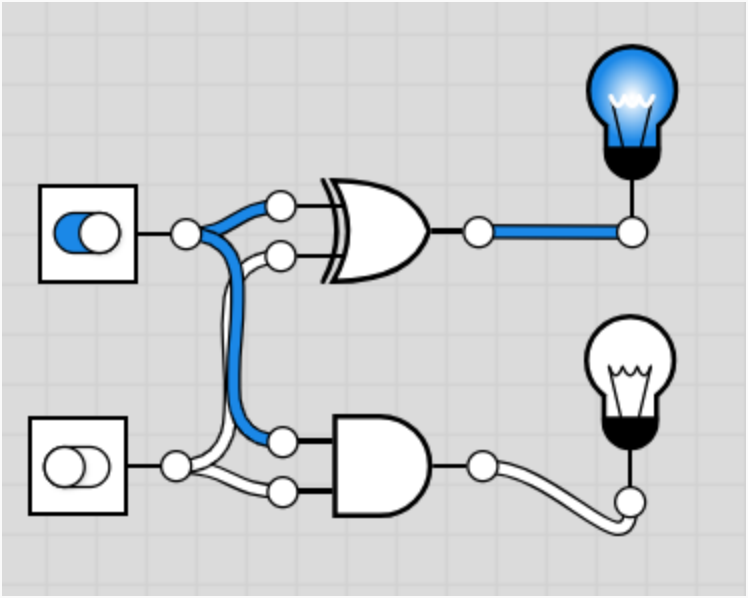

[PASS Hardware Simulator Screenshot for HalfAdder]

HDL --LBSt Project 2 HalfAdder

```
// and the book "The Elements of Computing Systems"
// by Nisan and Schocken, MIT Press.
// File name: projects/2/HalfAdder.hdl
/**
 * Computes the sum of two bits.
 */
CHIP HalfAdder {
    IN a, b;
    OUT sum,
        carry;

    PARTS:
    Xor(a=a, b=b, out=sum);
    And(a=a, b=b, out=carry);
}
```

Test Steps: 7 Outputs: 5 Slow Fast

Test Script | Compare File | Output File | Diff Table

```
set b 0,
eval,
output;

set a 1,
set b 1,
eval,
output;
```

Simulation successful: The output file is identical to the compare file


2.17 Chip: Full Adder (FullAdder.hdl)


- **Function:** Adds three 1-bit values (a, b, carry-in), producing sum and carry bits.
- **Interface:** Inputs: a, b, c (1-bit) | Outputs: sum, carry (1-bit)


```
CHIP FullAdder {
    IN a, b, c;
    OUT sum, carry;

    PARTS:
    HalfAdder(a=a, b=b, sum=s1, carry=c1);
    HalfAdder(a=s1, b=c, sum=sum, carry=c2);
    Or(a=c1, b=c2, out=carry);
}
```

[Logic Diagram]

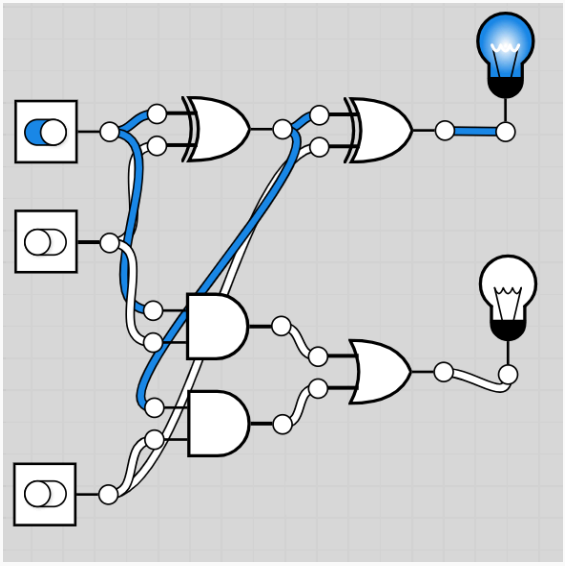

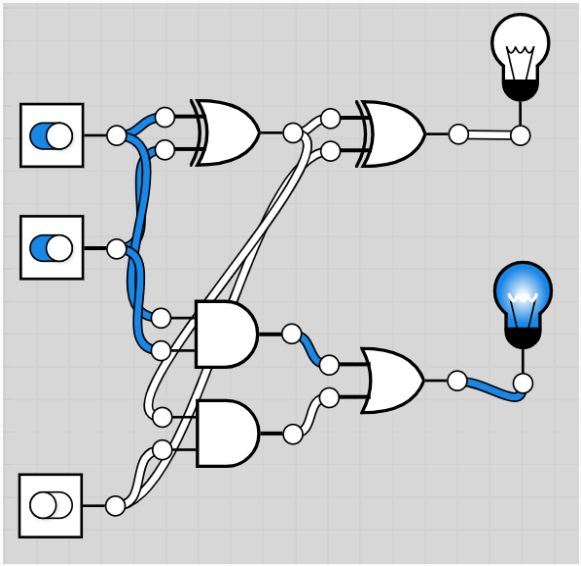

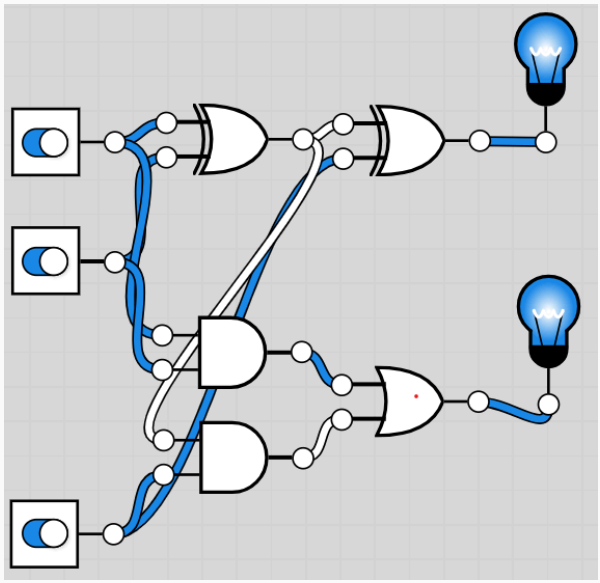

[PASS Hardware Simulator Screenshot for FullAdder]

HDL --LBSt Project 2 FullAdder

```
// by Nisan and Schocken, MIT Press.
// File name: projects/2/FullAdder.hdl
/**
 * Computes the sum of three bits.
 */
CHIP FullAdder {
    IN a, b, c;
    OUT sum,
        carry;

    PARTS:
    HalfAdder(a=a, b=b, sum=s1, carry=c1);
    HalfAdder(a=s1, b=c, sum=sum, carry=c2);
    Or(a=c1, b=c2, out=carry);
}
```

Test Steps: 11 Outputs: 9 Slow Fast

Test Script | Compare File | Output File | Diff Table

```
set b 1,
set c 0,
eval,
output;

set c 1,
eval,
output;
```

Simulation successful: The output file is identical to the compare file


2.18 Chip: 16-Bit Adder (Add16.hdl)

- **Function:** Adds two 16-bit 2's complement numbers.
- **Interface:** Inputs: a[16], b[16] | Outputs: out[16]


```
CHIP Add16 {
    IN a[16], b[16];
    OUT out[16];

    PARTS:
    HalfAdder(a=a[0], b=b[0], sum=out[0], carry=c0);
    FullAdder(a=a[1], b=b[1], c=c0, sum=out[1], carry=c1);
    FullAdder(a=a[2], b=b[2], c=c1, sum=out[2], carry=c2);
    FullAdder(a=a[3], b=b[3], c=c2, sum=out[3], carry=c3);
    FullAdder(a=a[4], b=b[4], c=c3, sum=out[4], carry=c4);
    FullAdder(a=a[5], b=b[5], c=c4, sum=out[5], carry=c5);
    FullAdder(a=a[6], b=b[6], c=c5, sum=out[6], carry=c6);
    FullAdder(a=a[7], b=b[7], c=c6, sum=out[7], carry=c7);
    FullAdder(a=a[8], b=b[8], c=c7, sum=out[8], carry=c8);
    FullAdder(a=a[9], b=b[9], c=c8, sum=out[9], carry=c9);
    FullAdder(a=a[10], b=b[10], c=c9, sum=out[10], carry=c10);
    FullAdder(a=a[11], b=b[11], c=c10, sum=out[11], carry=c11);
    FullAdder(a=a[12], b=b[12], c=c11, sum=out[12], carry=c12);
    FullAdder(a=a[13], b=b[13], c=c12, sum=out[13], carry=c13);
    FullAdder(a=a[14], b=b[14], c=c13, sum=out[14], carry=c14);
    FullAdder(a=a[15], b=b[15], c=c14, sum=out[15], carry=c15);
}
```

[Logic Diagram]

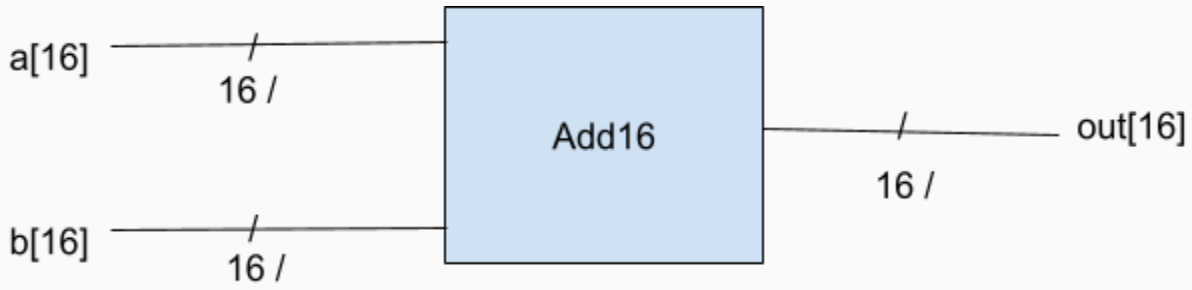

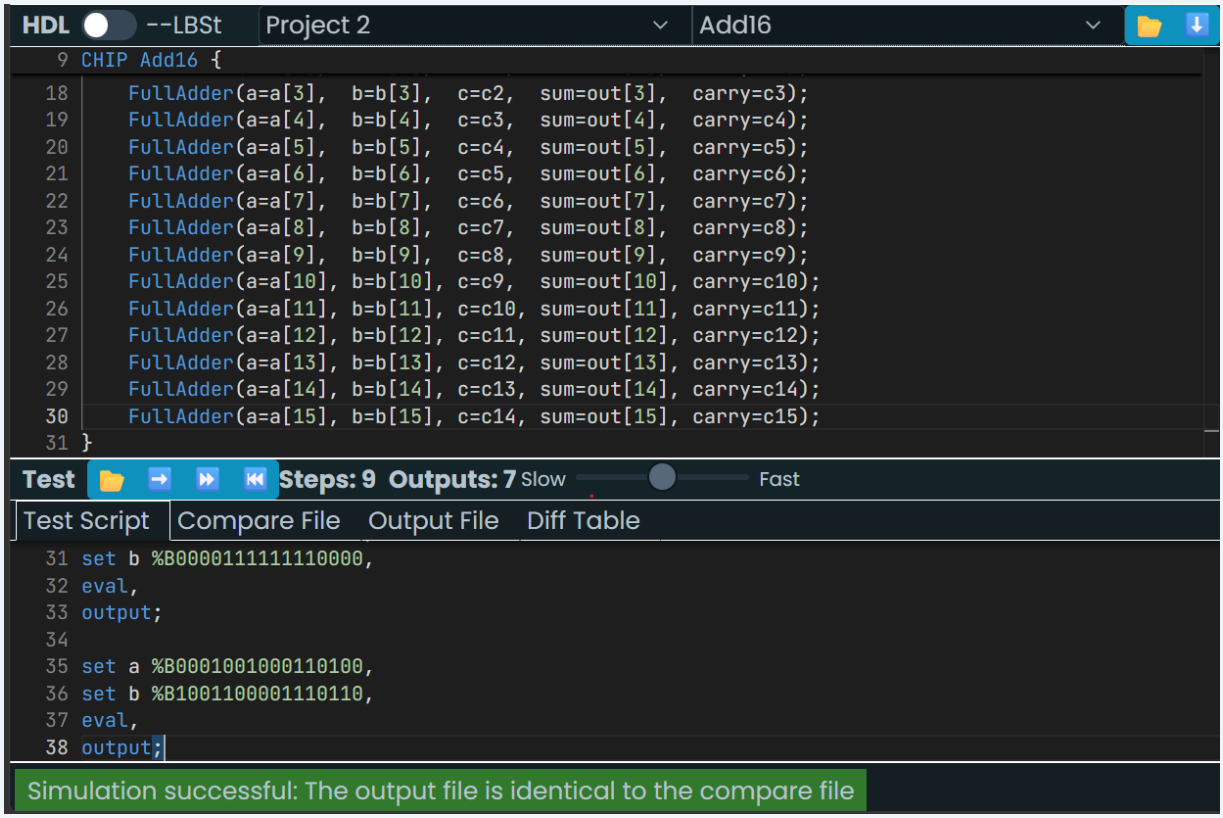[PASS Hardware Simulator Screenshot for Add16]



3. Section 3: Arithmetic Logic Unit (ALU)

The Hack Central Processing Unit (CPU) centers around a 16-bit Arithmetic Logic Unit (ALU). The ALU operates on two 16-bit inputs (x and y) and produces a 16-bit output controlled by six binary input bits (zx, nx, zy, ny, f, no). In addition to computing mathematical and logical functions, it yields two status flags: 'zr' (1 if output == 0) and 'ng' (1 if output < 0).

3.1 ALU HDL Implementation (ALU.hdl)

```
CHIP ALU {
    IN
        x[16], y[16], zx, nx, zy, ny, f, no;

    OUT
        out[16], zr, ng;

    PARTS:
    // Step 1: Handle zx and nx (zero/negate x)
    Mux16(a=x, b=false, sel=zx, out=x1);
    Not16(in=x1, out=nx1);
    Mux16(a=x1, b=nx1, sel=nx, out=x2);
```


```
    // Step 2: Handle zy and ny (zero/negate y)
    Mux16(a=y, b=false, sel=zy, out=y1);
    Not16(in=y1, out=ny1);
    Mux16(a=y1, b=ny1, sel=ny, out=y2);

    // Step 3: f - AND or ADD
    Add16(a=x2, b=y2, out=fAnd);
    And16(a=x2, b=y2, out=fAdd);
    Mux16(a=fAnd, b=fAdd, sel=f, out=fOut);


    // Step 4
    Not16(in=fOut, out=nfOut);
    Mux16(a=fOut, b=nfOut, sel=no, out=out, out[0..7]=low8, out[8..15]=high8,
out[15]=ng);

    // Step 5
    Or8Way(in=low8, out=orLow);
    Or8Way(in=high8, out=orHigh);
    Or(a=orLow, b=orHigh, out=notZero);
    Not(in=notzr, out=zr);
}
```

[Logic Diagram]

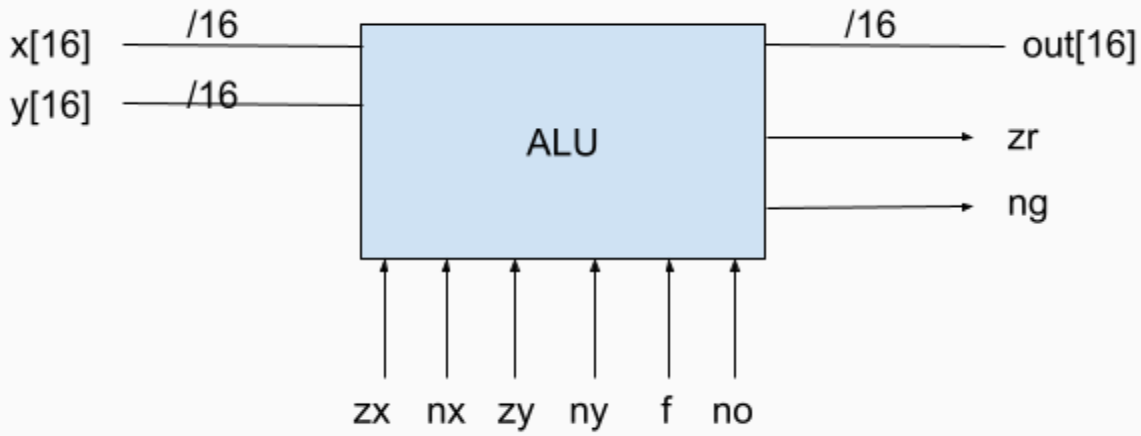

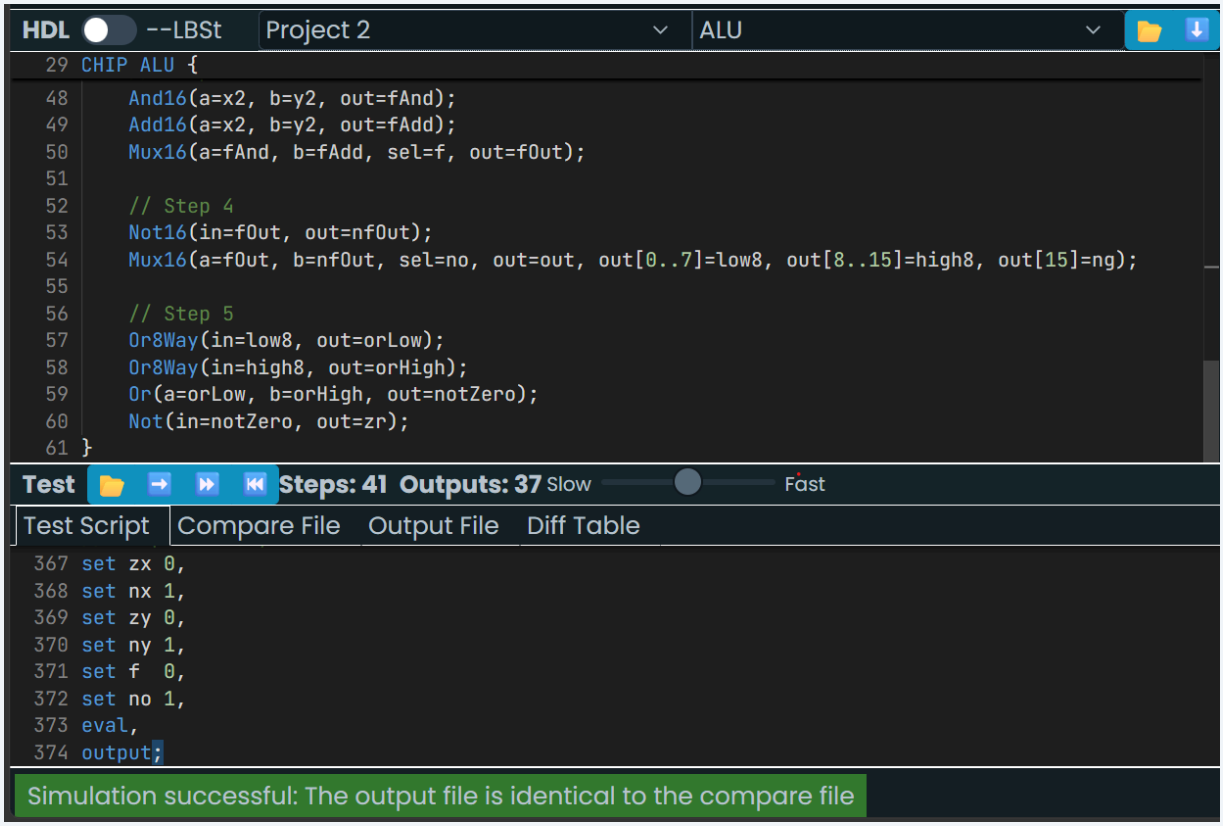[PASS Hardware Simulator Screenshot for ALU.hdl]



3.2 Comprehensive 17-Row ALU Function Truth Table

zx	nx	zy	ny	f	no	out	Function Description
1	0	1	0	1	0	**0**	Constant 0
1	1	1	1	1	1	**1**	Constant 1
1	1	1	0	1	0	**-1**	Constant -1
0	0	1	1	0	0	**x**	Input x
1	1	0	0	0	0	**y**	Input y
0	0	1	1	0	1	**!x**	Bitwise NOT x
1	1	0	0	0	1	**!y**	Bitwise NOT y
0	0	1	1	1	1	**-x**	Arithmetic Negate x
1	1	0	0	1	1	**-y**	Arithmetic Negate y
0	1	1	1	1	1	**x + 1**	Increment x
1	1	0	1	1	1	**y + 1**	Increment y
0	0	1	1	1	0	**x - 1**	Decrement x

1	1	0	0	1	0	**y - 1**	Decrement y
0	0	0	0	1	0	**x + y**	Addition
0	1	0	0	1	1	**x - y**	Subtraction
0	0	0	0	0	0	**x & y**	Bitwise AND
0	1	0	1	0	1	**x | y**	Bitwise OR

4. Section 4: Conclusion & Verification Summary Table

All 21 gate level and arithmetic modules for Project 1 and Project 2 were designed, implemented in Hardware Description Language (HDL), and systematically verified against standard test scripts (.tst) and expected output comparison tables (.cmp) in the NAND2Tetris Hardware Simulator. All chip tests completed successfully with zero output mismatches.

Project Module	Chip Name	Test Script File	Verification Status
Project 1: Elementary	Not	Not.tst	**PASS**
Project 1: Elementary	And	And.tst	**PASS**
Project 1: Elementary	Or	Or.tst	**PASS**
Project 1: Elementary	Xor	Xor.tst	**PASS**
Project 1: Elementary	Mux	Mux.tst	**PASS**
Project 1: Elementary	DMux	DMux.tst	**PASS**
Project 1: 16-Bit / Multi-Way	Not16	Not16.tst	**PASS**
Project 1: 16-Bit / Multi-Way	And16	And16.tst	**PASS**
Project 1: 16-Bit / Multi-Way	Or16	Or16.tst	**PASS**
Project 1: 16-Bit / Multi-Way	Mux16	Mux16.tst	**PASS**
Project 1: 16-Bit / Multi-Way	Or8Way	Or8Way.tst	**PASS**
Project 1: 16-Bit / Multi-Way	Mux4Way16	Mux4Way16.tst	**PASS**
Project 1: 16-Bit / Multi-Way	Mux8Way16	Mux8Way16.tst	**PASS**
Project 1: 16-Bit / Multi-Way	DMux4Way	DMux4Way.tst	**PASS**
Project 1: 16-Bit / Multi-Way	DMux8Way	DMux8Way.tst	**PASS**
Project 2: Arithmetic	HalfAdder	HalfAdder.tst	**PASS**
Project 2: Arithmetic	FullAdder	FullAdder.tst	**PASS**
Project 2: Arithmetic	Add16	Add16.tst	**PASS**
Project 2: Core Processing	ALU	ALU.tst	**PASS**